

NOR - pos  
NAAND - sop

3. (1) (12)

## UNIT - 2 (1-25)


Minimization of switching functions:

- The map method was proposed by Veitch  $\rightarrow$  This provides a simple straight forward procedure for simplification of Boolean fns.

The method is called Veitch Diag (or) Karnaugh map.  
- in 1952. It is a pictorial representation of a 2.2 (or) an extension of Venn diagram. & this is modified by M-Karnaugh in 1953. (K-map/Karnaugh map).

- K-maps can be implemented up to 5 (or) 6 variables but beyond it can be solved by using Quine-McCluskey method.

outline of 1, 2, 3, 4 variable K-map.

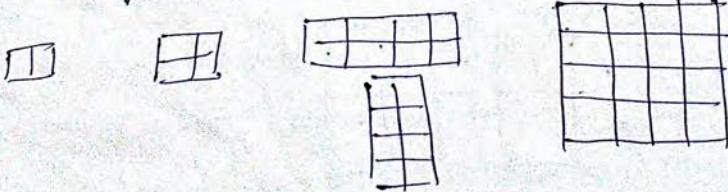

Representation of minterms on K-map.

A	B	$\bar{B}$	B
$\bar{A}$	$\bar{B}$	$\bar{B}$	AB
A	$\bar{B}$	AB	AB

2 variable.

A	$\bar{B} \bar{C}$	$\bar{B} C$	$B \bar{C}$	$B C$
$\bar{A}$	mo	m <sub>1</sub>	m <sub>3</sub>	m <sub>2</sub>
A	$\bar{A} \bar{B} \bar{C}$	$\bar{A} \bar{B} C$	$A \bar{B} \bar{C}$	$A \bar{B} C$

3 variable

AB	$\bar{C} \bar{D}$	$\bar{C} D$	$C \bar{D}$	$C D$
$\bar{A} \bar{B}$	mo	m <sub>1</sub>	m <sub>3</sub>	m <sub>2</sub>
$\bar{A} B$	m <sub>4</sub>	m <sub>5</sub>	m <sub>6</sub>	m <sub>7</sub>
AB	m <sub>8</sub>	m <sub>9</sub>	m <sub>11</sub>	m <sub>10</sub>
$A \bar{B}$	m <sub>7</sub>	m <sub>6</sub>	m <sub>4</sub>	m <sub>5</sub>

4 Variable

### Representation of Max terms

	B	$\bar{B}$	B
A	0	1	0
	$M_0$	$M_1$	$M_2$
	$M_L$	$M_R$	$M_3$

2-variable

	$\bar{B}C$	$BC$	$B\bar{C}$	$B\bar{C}$	$\bar{B}\bar{C}$
A	0 0	0 1	0 1	1 1	1 0
	$M_0$	$M_1$	$M_2$	$M_3$	$M_L$
	$M_R$	$M_S$	$M_T$	$M_B$	$M_G$

3-variable

	0	1
	$M_0$	$M_1$
	$M_2$	$M_3$

2-variable

plotting a T.T on K-map

	A	B	F
0	0	0	0
0	0	1	1
1	0	1	1
1	1	0	0

	B	0	1
0	0	0	1
1	1	1	0

$$F(A,B) = \sum m(1,2)$$

	X	0
1	0	1
0	1	0

$$F(A,B) = \overline{m}(1,2)$$

plotting sop exp on K-map:

$$Ex: F = \bar{A}\bar{B}\bar{C} + \bar{A}BC + A\bar{B}\bar{C}$$

	$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$
0	1	0	1	0
0	0	0	0	1

plotting sop exp on K-map

$$f = (A+B+C)(A+\bar{B}+C)(\bar{A}+B+C)(A+B+\bar{C}) = \overline{m}(0,1,2,5)$$

	$B\bar{C}$	$B\bar{C}$	$B\bar{C}$	$\bar{B}C$
$\bar{B}C$	0	0	1	0
$B\bar{C}$	1	0	1	1
$\bar{B}C$	0	1	0	1
$B\bar{C}$	1	1	1	0

s Max terms

Grouping of cells for minimized exp:

- Grouping horizontally
- Grouping vertically



Eg) pairing, quad, octal & so on.

summary of literals eliminated for n-variable K-map.

No. of 1's grouped	No. of literals eliminated	No. of literals present in resulting term.
6 (2 <sup>3</sup> )	6	n-6
8 (2 <sup>3</sup> )	5	n-5
16 (2 <sup>4</sup> )	4	n-4
8 (2 <sup>3</sup> )	3	n-3
4 (2 <sup>2</sup> )	2	n-2
2 (2 <sup>1</sup> )	1	n-1
1 2 <sup>0</sup>	0	n-0 = n


Eg: 3 variable K-map.

- No. of 1's grouped:  $2^3 \text{ i.e. } 8. 2 = 2^1$

- No. of literals eliminated: 2. 1

- No. of literals present in resulting term:  $n-8/1 = 3-1 = 2$
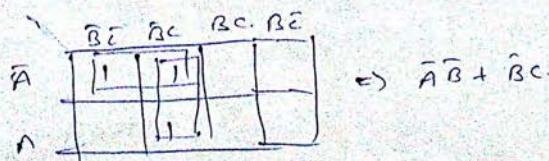
$$f = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}C$$



Prime Implicants & Essential Prime Implicants:  
 set of adjacent minterms / simplified product term  
 obtained by the minterms of sets.

P.I. → Implicant is called P.I. if it is not a subset of another implicant of the fun.

E.P.I. → A P.I. which includes a '1' cell that is not included in any other P.I.

$$\text{Ex: i) obtain E.P.I. of } f(A,B,C) = \Sigma m(1,3,4,15)$$

$$\begin{array}{c|cc|cc|c} & \bar{B}\bar{C} & \bar{B}C & BC & B\bar{C} \\ \bar{A} & 0 & 1 & 1 & 2 \\ \hline A & 1 & 1 & 1 & 0 \\ \bar{B} & 0 & 1 & 1 & 1 \\ \hline & 1 & 1 & 1 & 1 \end{array} \Rightarrow \bar{A}C + \bar{A}\bar{B} + \bar{B}\bar{C}$$

all 1's are covered - E.P.I.  
 so  $\bar{B}\bar{C}$  is not required.

$$\text{ii) } f(A,B,C,D) = \Sigma m(0,5,7,8,9,10,11,14,15)$$

$$\begin{array}{c|cc|cc|cc|c} & \bar{D}\bar{C} & \bar{D}C & DC & C\bar{D} \\ \bar{A}\bar{B} & 1 & & & 2 \\ \hline \bar{A}B & & 1 & 1 & \\ B & & 1 & 1 & 1 \\ \hline AB & 12 & 13 & 14 & 15 \\ \hline A\bar{B} & 1 & 1 & 1 & 1 \\ \bar{B} & 8 & & & 16 \end{array} = A\bar{B} + AC + \bar{C}\bar{D}\bar{B} + \bar{A}\bar{B}D$$

~~$+ \bar{C}B\bar{D}$~~   $\rightarrow \cancel{\bar{C}B\bar{D}}$   
 BCD is covered by  $\bar{A}B$  & AC.

$\therefore$  E.P.I. are all the 4.

Ex: 1.  $Y = A\bar{B}C + \bar{A}\bar{B}C + A\bar{B}C + A\bar{B}\bar{C} + A\bar{B}\bar{C}$

		$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$	
		1	1	1		
		A				

$$Y = \bar{B} + \bar{B}C$$

Minimal pos form using K-map:

1.  $Y = (A+B+\bar{C})(A+\bar{B}+\bar{C})(\bar{A}+\bar{B}+\bar{C})(\bar{A}+B+C)(\bar{A}+B+\bar{C})$

		$\bar{B}C$	$B\bar{C}$	$B\bar{C}$	$B\bar{C}$	$B\bar{C}$	
		$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$	$B\bar{C}$	
		A	1	0	0	1	

$$Y = (A+\bar{B})(B+\bar{C})(B\bar{C}) / (\bar{B}+C)(\bar{B}+\bar{C})$$

$$\bar{F}_G = (\bar{B})$$

$$F_G = \bar{B}C + BC + AC + BC$$

$$\bar{B}\bar{C} + AB + BC$$

Conversion of SOP to POS using K-map:

Ex: 1)  $f: \bar{B}\bar{C} + \bar{A}\bar{B} + ABC$

		$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$	
		$\bar{B}\bar{C}$	0	1	1	
		A	1	0	1	0

$$\bar{f}: \bar{B}C + AB\bar{C}$$

$$f = (B+\bar{C})(\bar{A}+\bar{B}+C)$$

2)  $f: \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + AB\bar{C} + ABC$  into POS form

		$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$		
		$\bar{B}\bar{C}$	1	1	0	1	
		A	1	0	1	1	

$$\bar{f} = \bar{A}B\bar{C} + A\bar{B}C$$

$$\therefore f = (A+\bar{B}+C)(\bar{A}+\bar{B}+\bar{C})$$

$$= \bar{C} + \bar{A}\bar{B} + AB$$

$$= (A+\bar{B}+\bar{C})C$$

3) conversion of pos to sop form using K-map.

$$F = (\bar{A} + \bar{B} + \bar{E}) (\bar{A} + B + E) \Rightarrow f = \bar{A}\bar{B}\bar{C} + A\bar{B}C$$

	$\bar{B}\bar{E}$	$\bar{B}C$	$BC$	$B\bar{E}$
$\bar{A}$	1	1	0	1
A	1	0	1	1

$$f = \bar{E} + \bar{A}\bar{B} + AB$$

— don't care combinations:

	A	B	C	f
0	0	0	1	
0	0	1		1
0	1	0		0
0	1	1		0
1	0	0		1
1	0	1		x
1	1	0		x
1	1	1		x

	$\bar{B}\bar{E}$	$\bar{B}C$	$BC$	$B\bar{E}$
$\bar{A}$	1	1	0	0
A	1	x	x	x

$$x < 0 \\ f = \bar{B}$$

$$4. f(A, B, C) = \sum m(0, 1, 5) + \sum d(4, 7)$$

	$\bar{B}\bar{C}$	$\bar{B}C$		
$\bar{A}$	1	1	3	2
A	x	1	x	1

$$f = \bar{B}$$

5 Redefine K-map in pos form

$$f(A, B, C, D) = \overline{\text{IM}}(0, 2, 6, 8, 12) + \overline{\text{ID}}(3, 4, 7, 10, 14)$$

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0	1	$x_3$	$\bar{x}_2$
$\bar{A}B$	$x_4$	5	$x_2$	0
$A\bar{B}$	0	12	13	15
$A\bar{D}$	0	8	9	11

$$f_1 = \bar{D}$$

$$f_2 = D$$

5-variable K-map:

		DE		V2	
		00	01	11	10
ABC		00	1	0	0
w	x	00	1	0	0
01	01	1	0	1	0
11	11	0	1	1	0
10	10	1	1	0	1

		DE		V2	
		00	01	11	10
ABC		00	1	1	1
v	z	00	1	1	1
01	01	1	1	1	1
11	11	1	1	1	1
10	10	1	1	1	1

$$V = 0 = \bar{A}$$

$$V = 1 = A$$

$$\text{ex: } f(A,B,C,D,E) = \sum m(0, 5, 6, 8, 9, 10, 11, 16, 20, 24, 25, 26, 27, 29, 31)$$

$$a: \bar{B}\bar{E}F\bar{D}E = \bar{B}\bar{E}F\bar{D}E = \bar{B}\bar{C}\bar{C}\bar{B}\bar{D}E$$

$$b: (8, 9, 10, 11, 24, 25, 26, 27) = B\bar{C}$$

$$c: (25, 27, 29, 31) = ABE$$

$$d: 5 \Rightarrow \bar{A}\bar{B}C\bar{D}E$$

$$e: 6 \Rightarrow \bar{A}\bar{B}CD\bar{E}$$

$$f: 16, 20 \Rightarrow A\bar{B}\bar{D}\bar{E}$$

$$f = B\bar{C} + \bar{C}\bar{D}\bar{E} + ABE + A\bar{B}\bar{D}\bar{E} + \bar{A}\bar{B}C\bar{D}\bar{E} + \bar{A}\bar{B}CD\bar{E}$$

$$6\text{-variable K-map: } f = \sum m(0, 3, 4, 5, 7, 8, 12, 13, 20, 21, 28, 29, 31, 24, 35, 38, 39, 42, 45, 46, 50, 54, 58, 61, 62, 63).$$

		EF		EF		EF	
		$\bar{E}\bar{F}$	$\bar{E}F$	$E\bar{F}$	$EF$	$\bar{E}\bar{F}$	$\bar{E}F$
$\bar{E}D$		1	0	1	0	1	2
$\bar{E}D$		1	1	1	0	1	6
$ED$		1	1	1	1	1	1
$ED$		2	12	13	15	14	10
$CD$		1	8	9	11	10	16
$CD$		0	4	5	7	6	11

$$A=0 \quad B=0$$

		EF		EF		EF	
		$\bar{E}\bar{F}$	$\bar{E}F$	$E\bar{F}$	$EF$	$\bar{E}\bar{F}$	$\bar{E}F$
$\bar{E}D$		1	1	1	1	1	1
$\bar{E}D$		1	1	1	1	1	1
$ED$		1	1	1	1	1	1
$ED$		2	20	21	23	24	26
$CD$		1	22	22	27	20	28
$CD$		0	24	26	20	22	26

$$A=0 \quad B=1$$

	32	33	1	1
	34	35	1	1
A	1	0	1	0
B	0	1	0	1
C	0	0	0	1
D	0	0	1	0
E	0	0	0	0
F	1	1	1	1

	32	33	1	1
	34	35	1	1
A	1	0	1	0
B	0	1	0	1
C	0	0	0	1
D	0	0	1	0
E	0	0	0	0
F	1	1	1	1

$$A = 1 \quad B = 1$$

$$A = x_1, B = x_2, C = x_3, D = x_4, E = x_5 \\ F = x_6$$

$$a = 3, 2, 1, 35, 33 \quad \bar{AB} \bar{C} \bar{E} \bar{F} = \bar{x}_1 \bar{x}_2 \bar{x}_3 \bar{x}_5 \bar{x}_6$$

$$b = 27, 31, 61, 63 \quad \bar{B} \bar{C} D \bar{E} \bar{F} = \bar{x}_2 \bar{x}_3 \bar{x}_4 \bar{x}_5 \bar{x}_6$$

$$c = 0, 4, 8, 12 \quad \bar{A} \bar{B} \bar{E} \bar{F} = \bar{x}_1 \bar{x}_2 \bar{x}_5 \bar{x}_6$$

$$d = 34, 38, 42, 46, 50, 54, 58, 62 \quad A \bar{C} \bar{F} = \bar{x}_1 \bar{x}_3 \bar{x}_5 \bar{x}_6$$

$$e = 4, 5, 12, 13, 20, 21, 28, 29 \quad \bar{E} D \bar{A} = \bar{x}_1 \bar{x}_4 \bar{x}_5$$

$$f = 45, 61, 13, 29 \quad \bar{E} \bar{F} C D = \bar{x}_5 \bar{x}_6 \bar{x}_3 \bar{x}_4$$

$F = a + b + c + d + e + f$

### Advantages of K-map:

- adv: 1. fast method of simplifying expression up to 4 variables
- 2. It gives visual method of logic simplification.
- 3. P.I & E.P.I can be easily identified.
- 4. This principle has been extended to VLSI design by incorporating it in the pass transistor logic design method.
- 5. suitable for both SOP & POS form for reduction.

disadv:

1. More the no. variables it is difficult to execute.
2. It is not suitable for computer deduction.

so

\* Tabular Method: Quine-Mccluskey Method:

- Binary Representation Method.
  - Decimal Representation Method.
1. Binary Representation Method:

Ex:  $f(A, B, C, D) = \sum m(0, 2, 3, 6, 7, 8, 10, 12, 13)$

1. list all the minterms in binary form & arrange them in the form of groups according to the no. of 1's contained

minterms	Binary Representation				No. of 1's	Index	Minterm	Binary rep.
	A	B	C	D				A B C D
$m_0$	0	0	0	0	0	0	$m_0 \swarrow$	0 0 0 0
$m_2$	0	0	1	0	1	1	$m_2 \swarrow$	0 0 1 0
$m_3$	0	0	1	1	2	2	$m_3 \swarrow$	0 1 0 0
$m_6$	0	1	1	0	2	2	$m_3 \swarrow$	0 0 1 1
$m_7$	0	1	1	1	3		$m_6 \swarrow$	0 1 1 0
$m_8$	1	0	0	0	1		$m_{12} \swarrow$	1 0 0 0
$m_{10}$	1	0	1	0	2	3	$m_9 \swarrow$	1 0 1 0
$m_{12}$	1	1	0	0	2		$m_{12} \swarrow$	1 1 0 0
$m_{13}$	1	1	0	1	3		$m_{13} \swarrow$	1 1 0 1

2. Compare each binary term with every term in the adjacent next higher category.  
 If they differ only by one position put a check mark and copy the term in to the next column, with  $\sim$  in the place where the variable is unmatched. Continue until no elimination of literals.

(ii) minterm      Binary Representation.

$m(0,2)$ ✓	0 0 - 0
$m(0,2)$ ✓	- 0 0 0
$m(2,3)$ ✓	0 0 1 -
$m(2,6)$ ✓	0 - 1 0
$m(8,10)$ ✓	- 0 1 0
$m(8,10)$ ✓	1 0 - 0
$m(8,12)$ P	1 - 0 0
$m(3,7)$ ✓	0 - 1 1
$m(6,7)$ ✓	0 1 1 -
$m(12,13)$ S	1 1 0 -

1 ii)  $m(0,2,8,10)$        $\sim 0 - 0$  R

$m(2,3,6,7)$       0 - 1 - S.

3. ~~Given~~ P.I are P, Q, R, S.

4. List all P.S in P.S table.

P.I	Binary Rep	LITERAL Rep.
$m(8,12)$	$ABCD$ $1 - 0 \ 0$	$A\bar{C}\bar{D}$
$m(12,13)$	$1 \ 1 \ 0 \ -$	$AB\bar{C}$
$m(5,2,8,10)$	$- \ 0 \ - \ 0$	$\bar{B}\bar{D}$
$m(2,3,6,7)$	$0 \ - \ 1 \ -$	$\bar{A}C$

- (ii) Now select EPJ i.e. min no. of P.I which must cover all the minterms using P.I chart (FBD)

Labels	P.I	LITERAL Rep	Minterms
P	2,12	$\bar{A}\bar{C}\bar{B}$	$m_0 \ m_2 \ m_3 \ m_6 \ m_7 \ m_8 \ m_{10} \ m_{12} \ m_{13}$
Q	13,13	$ABC$	$m_1 \ m_5 \ m_9 \ m_{11}$
R	5,2,6,10	$\bar{B}\bar{D}$	$m_3 \ m_7 \ m_{11} \ m_{13}$
S	2,3,6,7	$\bar{A}C$	$m_4 \ m_5 \ m_6 \ m_7$

Here  $m_0, m_3, m_6, m_7, m_{10}, m_{13}$  contains only 'x' & their corresponding P.I must be included in minimal sum as they are called EPJ

∴ Here Q, R, S are EPJ

These 3 EPJ are covering all minterms  
minimal expressions  $\therefore$

$$f = Q + R + S$$

$$= ABC + \bar{B}\bar{D} + \bar{A}C$$

Ex: 2.  $f(A, B, C, D) = \sum m(0, 1, 2, 5, 7, 8, 9, 10, 13, 15)$ .

(7)

	min terms	Binary	No. of 1's	Index	min terms	Binary
	A B C D				m <sub>0</sub>	A B C D
	0 0 0 0		0	0	m <sub>0</sub>	0 0 0 0
m <sub>0</sub>	0 0 0 0		0	0	m <sub>1</sub>	0 0 0 1
m <sub>1</sub>	0 0 0 1		1	1	m <sub>2</sub>	0 0 1 0
m <sub>2</sub>	0 0 1 0		1		m <sub>8</sub>	1 0 0 0
m <sub>5</sub>	0 1 0 0		2	2	m <sub>5</sub>	0 1 0 1
m <sub>7</sub>	0 1 1 1		3		m <sub>9</sub>	1 0 0 1
m <sub>8</sub>	1 0 0 0		1		m <sub>10</sub>	1 0 1 0
m <sub>9</sub>	1 0 0 1		2		m <sub>12</sub>	0 1 1 1
m <sub>10</sub>	1 0 1 0		2		m <sub>13</sub>	1 1 0 1
m <sub>13</sub>	1 1 0 1		3			
m <sub>15</sub>	1 1 1 1		4.			

	min terms	Binary	min terms	Binary
	A B C D		A B C D	
m(0, 1)	0 0 0 -	✓	m(0, 1, 8, 9)	P - 0 0 -
m(0, 2)	0 0 - 0	✓	m(0, 2, 8, 9)	0 - 0 - 0
m(0, 8)	- 0 0 0	✓	m(0, 8, 11, 9) m(0, 8, 2, 10)	B - 0 0 - B - D + 0
m(1, 5)	0 - 0 1	✓	m(1, 5, 9, 13)	R { - - 0 1
m(1, 9)	- 0 0 1	✓	m(1, 9, 5, 13)	R { - - 0 1
m(2, 10)	- 0 1 0 P	✓		
m(8, 9)	1 0 0 -	✓	m(5, 7, 13, 15)	S { - 1 - 1
m(8, 10)	1 0 - 0	✓	m(5, 13, 7, 15)	S { - 1 - 1
m(5, 7)	0 1 - 1	✓		
m(5, 13)	- 1 0 1	✓		
m(9, 13)	1 - 0 1	✓		
m(7, 15)	- 1 1 1	✓		
m(13, 15)	1 1 - 1	✓		

min terms

Prime Implicants

$m(0,1,8,9) P$

$m(0,2,8,10) Q$

$m_0 m_2 m_8 m_{10} C \text{ or } Q$

$m(1,5,9,13) R$

$m(5,7,13,15) S$

A B C D  
Binary representation

- 0 0 -

- 0 - 0

~~0 0 0 0~~

- - 0 1

- 1 - 1

LITERAL Representation

$\bar{B} \bar{C}$

$\bar{B} \bar{D}$

$\bar{C} D$

$B D$

4) EPS  $\rightarrow$  no. of PI which must cover all minterms from

PI's shown:

P.I.	PI minterms	literal	$m_0$	$m_1$	$m_2$	$m_3$	$m_4$	$m_5$	$m_6$	$m_7$	$m_8$	$m_9$	$m_{10}$	$m_{11}$	$m_{12}$	$m_{13}$	$m_{14}$	$m_{15}$
P	0,1,8,9	$\bar{B} \bar{C}$	x	x								x	x					
Q	0,2,8,10	$\bar{B} \bar{D}$	x		(x)						x		(x)			x		
R	1,5,9,13	$\bar{C} D$		x		x						x				x		
S	5,7,13,15	$B D$				x	(x)									x	(x)	

$m_2 \in m_{10}$  is covered by only one P.I. Q }  $\rightarrow$  EPS

$m_5 \in m_{15}$  from P.I. S

By using Q & S the minterms covered are

0, 2, 8, 10, 5, 7, 13, 15

The two EPS cover all minterms except 1, 9

These can be covered by using either P (or) R.

$\therefore$  minimal expression f = P + Q + S (or) R + Q + S.

$\therefore f = \bar{B} \bar{C} + \bar{B} \bar{D} + B D$  (or)  $\bar{B} \bar{D} + \bar{C} D + B D$

(6) Implicant :  $\begin{array}{c} 0000 \\ 0010 \\ \Rightarrow 00-0 \end{array}$  This term is called implicant.  
dy: from the above the implicant can be used to express.

the two other terms.  
(ie)  $\bar{A}\bar{B}\bar{D}$  is used instead  $\bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D}$

prime implicants : The terms that did not match clearing the process is called P.I.

Ex: McClellan's method :

$$F(A,B,C,D) =$$

$$\Sigma m(1,2,3,5,9,12,14,15) + \Sigma d(4,8,11)$$

$$Y(w,x,y,z) = \Sigma m(1,2,3,5,9,12,14,15) + \Sigma d(4,8,11)$$

minterms	Binary exp index minterms	Binary Rep.
1	$\begin{array}{c} 0000 \\ 0001 \\ 0010 \\ 0011 \end{array}$	$\begin{array}{c} 0000 \\ 0001 \\ 0010 \\ 0011 \end{array}$
2	$\begin{array}{c} 0010 \\ 0011 \\ 0100 \end{array}$	$\begin{array}{c} 0010 \\ 0011 \\ 0100 \end{array}$
3	$\begin{array}{c} 0011 \\ 0100 \end{array}$	$\begin{array}{c} 0011 \\ 0100 \end{array}$
5	$\begin{array}{c} 0100 \\ 1001 \end{array}$	$\begin{array}{c} 0100 \\ 1001 \end{array}$
9	$\begin{array}{c} 1100 \\ 1110 \end{array}$	$\begin{array}{c} 1100 \\ 1110 \end{array}$
12	$\begin{array}{c} 1110 \\ 1111 \end{array}$	$\begin{array}{c} 1110 \\ 1111 \end{array}$
14	$\begin{array}{c} 1111 \\ 0100 \end{array}$	$\begin{array}{c} 1111 \\ 0100 \end{array}$
15	$\begin{array}{c} 0100 \\ 1000 \end{array}$	$\begin{array}{c} 0100 \\ 1000 \end{array}$
d 4	$1000$	
8	$1011$	
11		

minterms	Rep:	minterms	Binary
(1,3)	00-1✓	(3,11)	-011-
(1,5)	0-01	(9,11)	10-1-
(1,9)	-00 1✓	(13,14)	11-0-
(2,3)	001-	(11,15)	1-11
(4,5)	010-	(7,15)	111-
(4,12)	0100		
(2,9)	100-		
(8,12)	1-00		

List of PI

P.I	min	/ Binary rep.
$\bar{A}CD$	1,5	0 - 0 1
$\bar{A}\bar{B}C$	2,3	0 0 1 -
$\bar{A}\bar{B}\bar{C}$	4,6	0 1 0 -
$B\bar{C}\bar{D}$	4,12	- 1 0 0
$A\bar{B}\bar{C}$	8,9	1 0 0 -
$A\bar{C}\bar{D}$	8,12	1 - 0 0
$AB\bar{D}$	12,14	1 1 - 0
$AC\bar{B}$	11,15	1 - 1 1
$ABC$	14,15	1 1 1 -
$\bar{B}D$	1,3,9,11	- 0 - 1

12.5 Selection table,

P.I	$m_1$	$m_2$	$m_3$	$m_4$	$m_5$	$m_6$	$m_7$	$m_8$	$m_9$	$m_{10}$	$m_{11}$	$m_{12}$	$m_{13}$	$m_{14}$	$m_{15}$
(1,5) $\bar{A}CD$	x						x								
8,13 $\bar{A}\bar{B}C$				x	x										
4,15 $\bar{A}B\bar{C}$				x	x	x									
11,12 $B\bar{C}\bar{D}$				x								x			
8,9 $A\bar{B}\bar{C}$							x	x	x	x					
8,12 $A\bar{C}\bar{D}$							x	x			x				
12,14 $AB\bar{D}$											x	x			
11,15 $ACD$									x	x			x		
14,15 $ABC$										x			x	x	x
1,3,9,11 $\bar{B}D$	x			x				x		x					

$$Y = \bar{A}\bar{C}D + \bar{A}\bar{B}C + \bar{B}D + AB\bar{D} + ABC$$

Ex:  $f(A,B,C) = \sum m(0,1,2,5,6,7)$

min terms	Binary dep	min terms	min terms	Binary dep
0	000	0,1	0,1	00- = P
1	001	1	0,2	0-0 Q
2	010	2	1,5	-01 R
5	101	5	2,6	-10 S
6	110	6	5,7	1-1 T
7	111	7	6,7	11- U

P.I Selection table:

P.I	m <sub>0</sub>	m <sub>1</sub>	m <sub>2</sub>	m <sub>3</sub>	m <sub>4</sub>	m <sub>5</sub>
$\bar{A}\bar{B}$ P	0,1	*	*	*	*	*
$\bar{A}C$ Q	0,2	*	*	*	*	*
$\bar{B}C$ R	1,5	*	*	*	*	*
$B\bar{C}$ S	2,6	*	*	*	*	*
AC T	5,7	*	*	*	*	*
ABU	6,7	*	*	*	*	*

\* when each column in P.I Selection chart has two  $\Sigma$  mle dots, the chart is known as cyclic prime Implicant chart.

\* proceed by trial & error method.

one of the sol is  $\bar{A}\bar{B} + B\bar{C} + AC$ .

\* P.I which are not selected i.e. (0,2)(4,5)(6,7)

are called redundant P.I.

Petrie's method of determining irredundant Exp:

- from above Ex:

Exp covering a P.I table is represented by.

$$e = (P+Q)(P+R)(Q+S)(R+S)(S+U)(T+U)$$

$$\quad \quad \quad m_0 \quad m_1 \quad m_2 \quad m_3 \quad m_4 \quad m_5$$

$$\begin{aligned}
 (\because (A+B)(A+C) = A+B) \\
 A+BC &= (P+QR)(S+QR)(U+ST) \\
 &= (PS + PQR + SQR + QR)(U+ST) \\
 &= \underline{PSU} + \underline{PST} + \underline{PQRU} + \underline{PQRST} + \underline{SQRU} + \underline{SQRST} + \\
 &\quad \quad \quad \underline{QRU} + \underline{QRST}
 \end{aligned}$$

$P_{S0}$ 

$$= P.S.U + P.S.T + \underline{Q.R.U} + Q.R.S.T$$

$$f_1(A,B,C,D) = P+S+U$$

$$f_2(A,B,C,D) = P+S+T$$

$$f_3(A,B,C,D) = Q+R+U$$

$$\text{minimal sum is } \Rightarrow f_1 + f_2 + f_3$$

adv & dis of Quine-McCluskey method:

- This method is algorithmic in nature
- It is lengthy & time consuming as no. of variables n.

### Decimal Method for obtaining P.3:

$$Ex.: f = \Sigma m(2,4,5,9,12,13)$$

minterms arrangement

	2	4	5	9	12	13	(2,4,5,9,12,13)	(1,8)
	00101	01001	01011	10011	11001	11011	(1) 4,5	010 - ✓
	00101	01001	01011	10011	11001	11011	(2) 4,13	-10011
	00101	01001	01011	10011	11001	11011	(2) 5,13	-101
	00101	01001	01011	10011	11001	11011	(4) 9,13	1-01
	00101	01001	01011	10011	11001	11011	(1) 12,13	110 - ✓

P. I

P. I is - fsum.

2

0010

$\bar{A}\bar{B}C\bar{D}$

1-01

AED

9,13 (4)

-10-


$B\bar{C}$

4,5,12,13 (1,8)

## combinational logic design

when logic gates are connected together to produce a specified o/p for certain specified combinations of ip variables with no storage involved, the resulting circuit is called combinational logic. (here o/p variables are at all times dependent on ip variables).


Block dia. of combinational circuit.

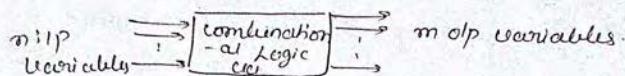

procedure to determine Boolean fun for o/p's of cel from given cel:

1. Make sure that given cel is comb cel & not degree cel.  
has logic gates with  
no feedback path (i.e)  
memory element.
2. Label all gate o/p's that are a fun of ip variables  
with arbitrary sym & determine Boolean fun for each gate o/p.
3. Label the gates that are a fun of ip variables &  
previously labelled gate & determine the B.fun for them.
4. Repeat step 3 until B.fun for o/p of the cel obtained  
finally sub previously defined B.fun, obtain the  
o/p of B.fun in terms of ip variables.

Q. obtain B-fun for o/p's of.

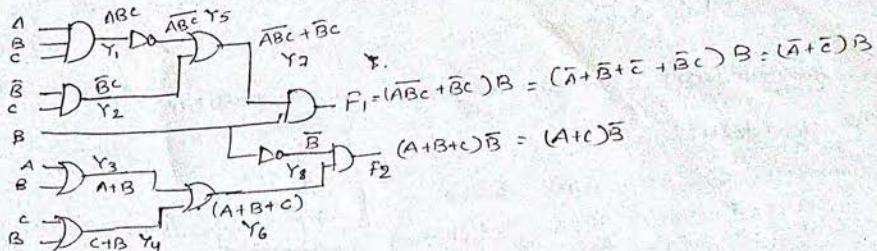

T-T!			$Y_1$	$Y_2$	$Y_3$	$Y_4$	$Y_5$	$Y_6$	$Y_7$	$Y_8$	$F_1$	$F_2$
A	B	C	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	1	0	0	0
0	1	0	0	0	1	0	0	1	1	0	0	0
0	1	1	0	0	0	1	0	0	1	1	0	0
1	0	0	0	0	0	0	1	0	0	0	0	0
1	0	1	0	1	1	0	0	1	1	1	0	0
1	1	0	0	0	0	1	0	0	1	1	0	0
1	1	1	1	0	1	0	1	0	1	1	0	0


simplified Boolean fun:

	$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$
$\bar{A}$	1	1	1	1
$\wedge$	1	1	1	1
$\bar{A}$	1	1	1	1
$\wedge$	1	1	1	1

T.T

$$f(A, B, C) = \sum m(1, 2, 3, 4, 5, 6)$$
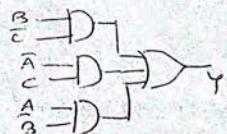
$$f(A, B, C) = BC + \bar{A}C + A\bar{B}$$




Adder:

$$\begin{array}{r} \begin{array}{c} \text{1} \\ \text{B} \\ \text{S} \\ \text{0} \end{array} \\ \begin{array}{c} \text{0} + \text{0} : \text{0} \\ \text{0} + \text{1} : \text{1} \\ \text{1} + \text{0} : \text{1} \\ \text{1} + \text{1} : \text{10} \end{array} \end{array}$$

T.T

Half adder:

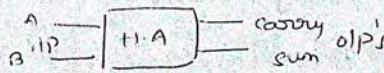

Block schematic


K-map:


	$\bar{B}$	$B$
$\bar{A}$	0	1
$A$	1	0

	$\bar{B}$	$B$
$\bar{A}$	0	0
$A$	0	1

$$C = AB$$

logic diagram


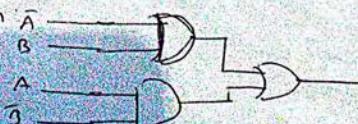


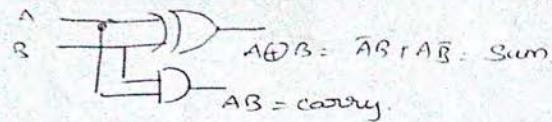


Limitations: 3 bit addition is not possible.

Full adder:

i/p's			o/p's		
A	B	cin	s	cout	β
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	0	1	0
1	1	0	0	1	0
1	1	1	1	1	1

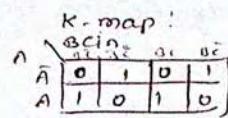
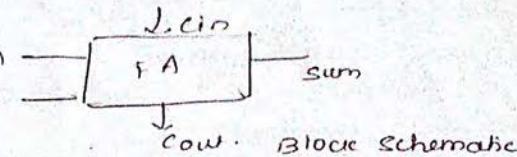

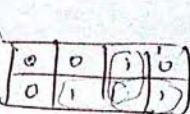
$$\text{sum} = \bar{A}\bar{B}\bar{\text{cin}} + \bar{A}\bar{B}\text{cin} + A\bar{B}\bar{\text{cin}} + AB\bar{\text{cin}}$$




$$\text{carry} = B\text{cin} + A\bar{B}\text{cin} + AB.$$

Logic dia:

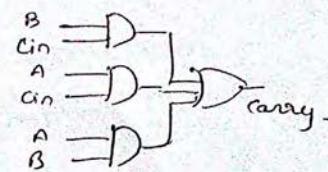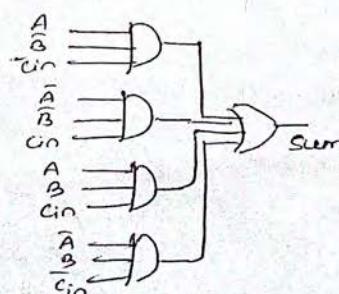


Simplification of sum:

$$\begin{aligned}
 & A\bar{B}\bar{\text{cin}} + \bar{A}\bar{B}\text{cin} + AB\text{cin} + \bar{A}B\bar{\text{cin}} \\
 &= \bar{B}\text{cin} [A + \bar{A}] + AB\text{cin} + \bar{A}B\bar{\text{cin}} \Rightarrow \bar{B}\text{cin} [\bar{A}\bar{B} + A\bar{B}] \\
 &+ \bar{\text{cin}} [\bar{A}\bar{B} + A\bar{B}] \\
 &= \text{cin} [\bar{B} + AB] + \bar{A}B\bar{\text{cin}} \\
 &= \text{cin} [\bar{B} + A] + \bar{A}B\bar{\text{cin}} \\
 &= A\text{cin} + \bar{B}\text{cin} + \bar{A}B\bar{\text{cin}} \\
 &\Rightarrow \bar{B}\text{cin} [\bar{A} \oplus B] + \bar{A}\text{cin} [\bar{A} \oplus B] \\
 &+ A\text{cin} [\bar{A} \oplus B] \\
 &\Rightarrow \text{cin} (\bar{A} \oplus B) + \bar{\text{cin}} (\bar{A} \oplus B) \\
 &\Rightarrow \text{cin} \oplus (\bar{A} \oplus B) + \bar{\text{cin}} \oplus (\bar{A} \oplus B) \\
 &\Rightarrow \text{cin} \oplus (\bar{A} \oplus B) + \bar{\text{cin}} \oplus (\bar{A} \oplus B) \\
 &\Rightarrow \text{cin} \oplus (\bar{A} \oplus B) + \bar{\text{cin}} \oplus (\bar{A} \oplus B)
 \end{aligned}$$

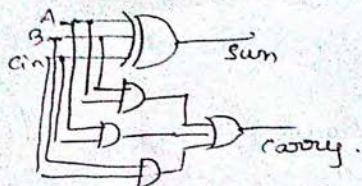

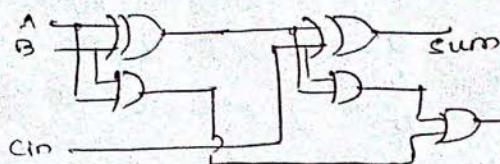Implementation of F.A. using two H.A.'s & OR gate:




$$\begin{aligned}
 &= BCin + ACin + AB \\
 &= AB + ACin + BGin(A + \bar{A}) \\
 &= AB + ACin + ABGin + \bar{A}BGin \\
 &= ACin + \bar{A}BCin + AB \\
 &= AB + ACin(B + \bar{B}) + \bar{A}BGin \\
 &= AB + ABCin + A\bar{B}Gin + \bar{A}BGin \\
 &= AB + Gin(\bar{A}B + \bar{A}B)
 \end{aligned}$$

Subtractors!

$$\begin{array}{l}
 0-0 = 0 \\
 0-1 = 1 \quad B = 1 \\
 1-0 = 1 \\
 1-1 = 0
 \end{array}$$


Half subtractor:

Inputs		Outputs	
A	B	Diff	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

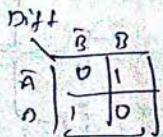


$$\text{Diff} : A\bar{B} + \bar{A}B$$

$$A \oplus B$$

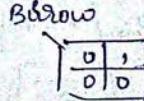

$$\text{Borrow} = \bar{A}B$$

Logic circuit:

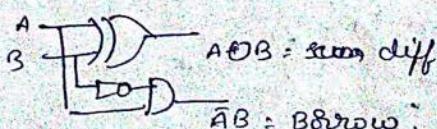

Full subtractor:

Inputs			Outputs	
A	B	Bin	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

D	$\bar{B}\bar{B}_{in}$	$\bar{B}\bar{B}_{in}$	$B\bar{B}_{in}$	$BB_{in}$
$\bar{A}$	0	1	0	1
A	1	0	1	0

Bout	0	1	0	1
0	0	1	0	0


$$D = \bar{A}\bar{B}\bar{B}_{in} + \bar{A}\bar{B}B_{in} + AB\bar{B}_{in} + AB\bar{B}_{in}$$

$$= \bar{B}_{in} [\bar{A}\bar{B} + \bar{A}B] + B_{in} [\bar{A}B + AB]$$


$$= \bar{B}_{in} [A \oplus B] + B_{in} [A \oplus B]$$

$$= \bar{B}_{in} [A \oplus B] + B_{in} [\overline{A \oplus B}]$$

$$= B_{in} \oplus (A \oplus B)$$

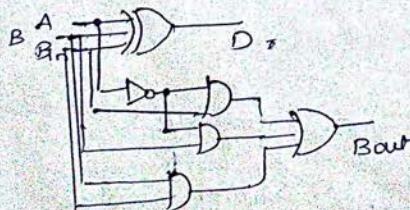
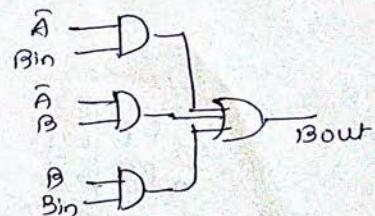
$$Bout = \bar{A}B_{in} + \bar{A}B + B\bar{B}_{in}$$



Implementation of full subtractor.

(12)

## Implementation of F-S using two H.S's. for gate.

$$B_{out} = \bar{A}B_{in} + \bar{A}B + BB_{in}$$

$$= \bar{A}B + \overline{B_{in}(\bar{A} + B)}$$

$$= \bar{A}B + \overline{B_{in}(\bar{A}\bar{B} + \bar{A}B)}$$

$$\Rightarrow \bar{A}B + \bar{A}B_{in}(B + \bar{B}) + BB_{in}$$

$$\Rightarrow \bar{A}B + \bar{A}BB_{in} + \bar{A}\bar{B}B_{in} + BB_{in}$$

$$\cancel{\bar{A}B + \bar{A}B B_{in} + \bar{A}\bar{B}B_{in}} + BB_{in} \Rightarrow \cancel{\bar{A}B} + \bar{A}\bar{B}B_{in} \neq \bar{A}B(B_{in}) + BB_{in}$$

$$\Rightarrow \bar{A}B + \bar{A}BB_{in} + B_{in}(\cancel{A + \bar{A}}) \Rightarrow \bar{A}\bar{B}B_{in} + \bar{A}B + BB_{in}$$

$$\Rightarrow \cancel{\bar{A}B + \bar{A}\bar{B}B_{in} + ABB_{in}} + \cancel{\bar{A}\bar{B}B_{in}} \Rightarrow \bar{A}\bar{B}B_{in} + B_{in}(A + \bar{A}) + \bar{A}B$$

$$= \bar{A}\bar{B}B_{in} + \bar{A}B + BB_{in} \Rightarrow \bar{A}\bar{B}B_{in} + AB + \bar{A}B$$


$$\Rightarrow \bar{A}\bar{B}B_{in} + ABB_{in} + \bar{A}B(1 + B_{in})$$

$$\Rightarrow \bar{A}\bar{B}B_{in} + ABB_{in} + \bar{A}B$$

$$\Rightarrow \bar{A}B + (AB + \bar{A}B)B_{in}$$

$$\Rightarrow \bar{A}B + \overline{(AB + \bar{A}B)}B_{in}$$
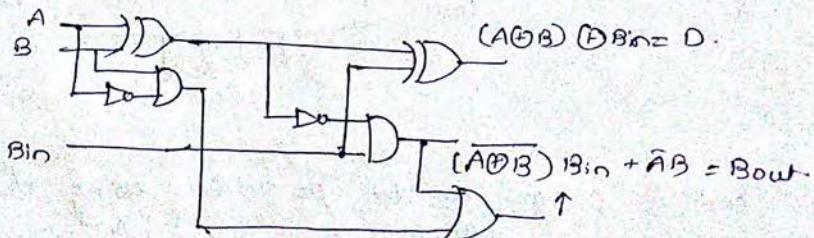
$$\Rightarrow \bar{A}B + \overline{(A \oplus B)}B_{in}$$




Ques 62, 63, 80, 81, 84, 86, 87, 89, 80, 83, 86, 891, 895, 96, 97, 98, 99

A<sub>1</sub>, A<sub>6</sub>, B<sub>1</sub>, B<sub>4</sub>

P1, A2


## Binary Adder / parallel Adder :

Block dia of nbit parallel adder.

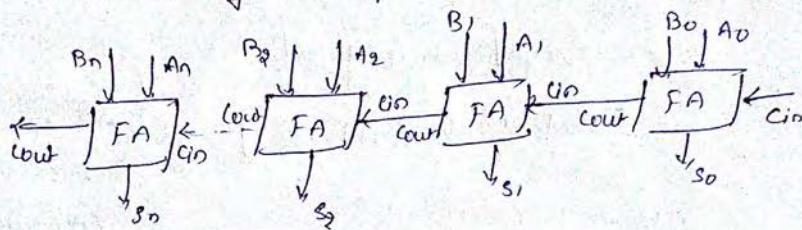


Note : carry = 0 bcz there is no carry into LSB position.

Ex: 4bit parallel adder using F.A.

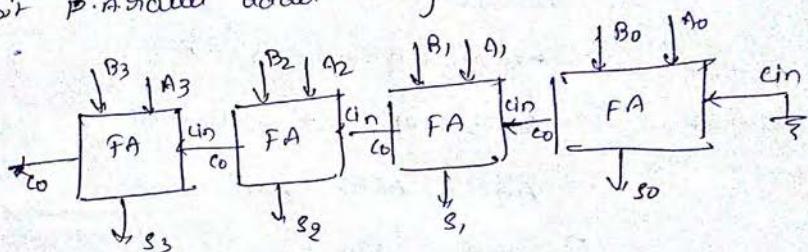


Block dia:

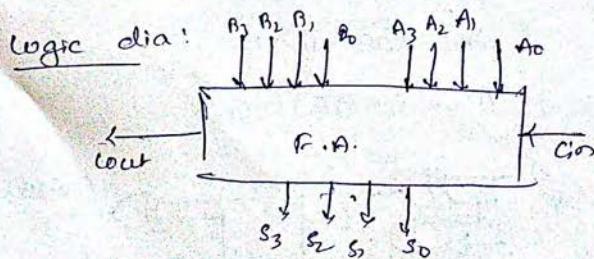

Binary parallel adder  
(IC 74LS83/  
74LS283)


(Functional sym.)

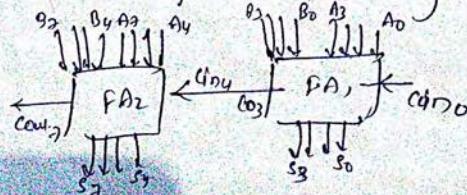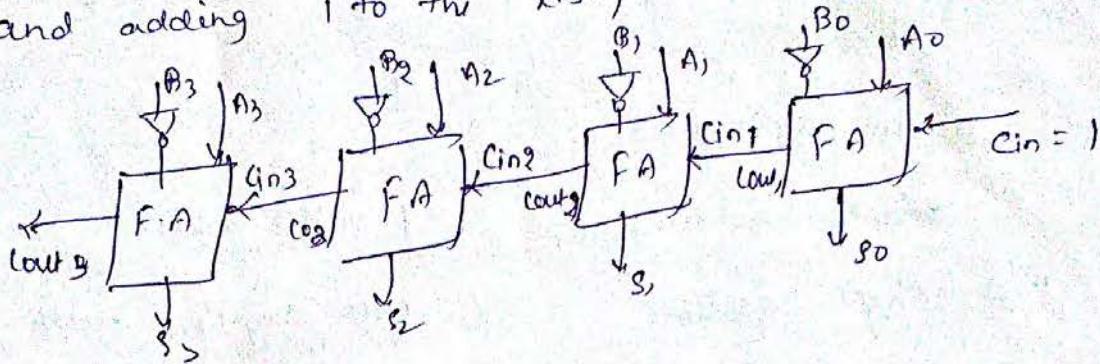Ex 2: design an 8bit pa adder using two 74283s.



Binary subtractor / parallel sub:

Here sub can be obtained by tracing 2's comp of - we no., 2's comp can be obtained by tracing 1's comp and adding 1 to the l.s. pair bit '1'.

Parallel adder/subtractor:

$M$ : Mode ilp controls the operation i.e. addition/sub.

$M=0$  = addition

$M=1$  = sub.

when  $M=0$ , one ilp is


each XOR gate receives  $ilp = M$   
 $\oplus$ 's  $ilp = B$

$$\text{addition} \Rightarrow (ie) \quad M=0 \Rightarrow M \oplus B \Rightarrow 0 \oplus B = 0\bar{B} + 1 \cdot B \\ \Rightarrow B \\ C_{in0} = 0$$

$$M=1 \Rightarrow M \oplus B \Rightarrow 1 \oplus B = 1\bar{B} + 0 \cdot B \\ \Rightarrow \bar{B} \\ C_{in0} = 1$$

it performs sub bcz

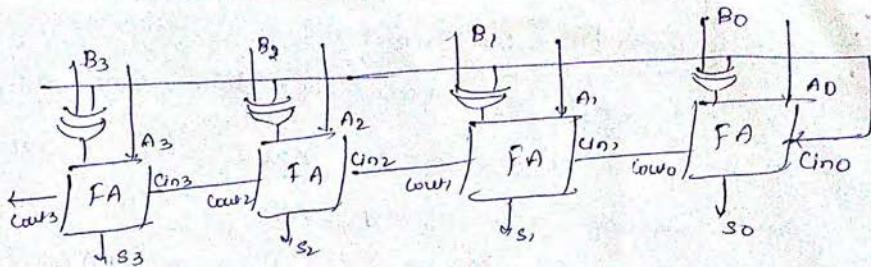B ilp's are all complemented & 1 is added.



### 4 bit addition - subtraction:

serial adder

parallel adder.

- 1. uses shift registers
- 1. uses registers with parallel load capacity
- 2. requires only 1 full adder circ.
- 2. No. of F.A. circ = no. of bits in the binary no.
- 3. It is sequential circ
- 3. Excluding reg, It is a purely combinational circ
- 4. Time required for addition depends on no. of bits
- 4. doesn't depend on no. of bits
- 5. It is slower
- 5. faster

### carry look ahead adder:

\* In parallel adder the higher bits are generated iff lower bits are added producing sum & carry


this results in delay called carry prop delay.

\* One method of speeding up the process by eliminating inter stage carry delay is look ahead carry addition

(14)

It uses two functions 1. carry generation  
2. carry propagation.

Full adder circuit:

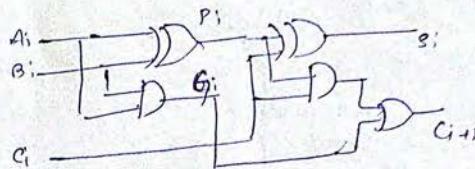

$$P_i = A_i \oplus B_i$$

$$G_i = A_i B_i$$

$$S_i = P_i \oplus C_i$$

$$C_{i+1} = P_i C_i + G_i$$

$C_1$

$$i=1, \quad C_2 = P_1 C_1 + G_1$$



$$C_3 = P_2 C_2 + G_2 = P_2 (P_1 C_1 + G_1) + G_2$$

$$= P_1 P_2 C_1 + P_2 G_1 + G_2$$

$$C_4 = P_3 C_3 + G_3$$

$$= P_3 P_2 P_1 C_1 + P_3 P_2 G_1$$


$$+ P_3 G_2 + G_3$$

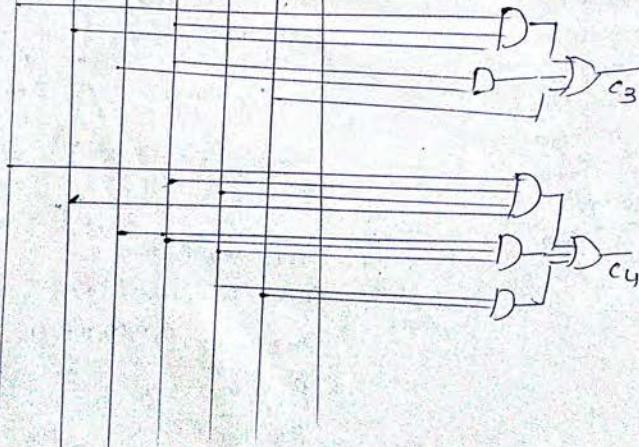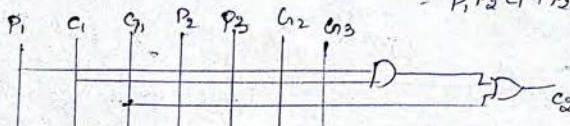


from above it is clear that  $C_4$  ~~has~~ doesn't have to wait until generation of  $C_2$  &  $C_3$ .

4. List parallel adder with a look-ahead


Carry Scheme.

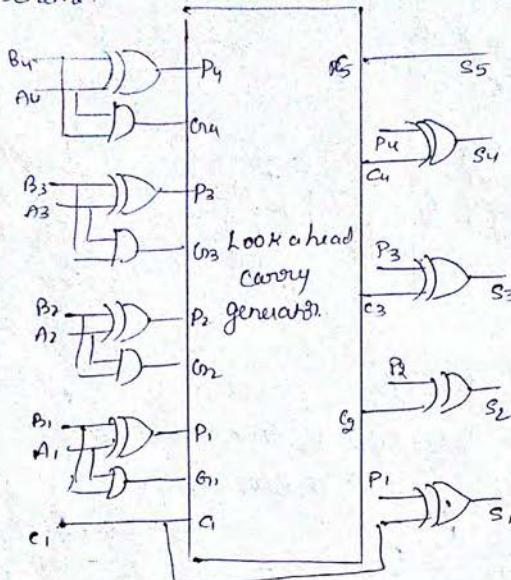

Logic Sym:

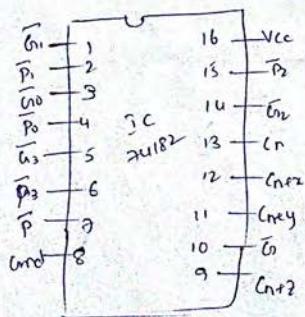

Pin dia.

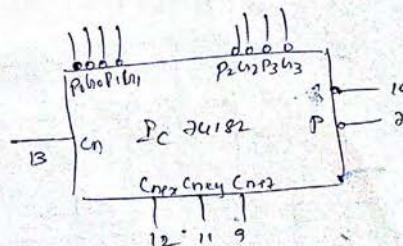

$$C_{n+2} = G_0 + P_0 \bar{G}_n$$

$$C_{n+4} = G_1 + P_1 G_0 + P_1 P_0 \bar{G}_n$$

$$C_{n+6} = G_2 + P_2 P_1 G_0 + P_2 G_1$$

$$\bar{G} = \overline{(G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0)}$$

$$\bar{P} = \overline{P_3 P_2 P_1 P_0}$$

Decimal adder:

BCD addition:

1. add two no.s
2.  $\leq 9 \Rightarrow$  no correction
3.  $> 9 \Rightarrow C=1$ , sum invalid.  
then add 0110 to 4bit sum if carry = 1 again add it to the next higher order BCD digit.

1lp's

$s_3$	$s_2$	$s_1$	$s_0$	1lp's
0	0	0	0	0
0	0	0	1	1
0	0	1	0	10
0	0	1	1	11
0	1	0	0	10
0	1	0	1	11
0	1	1	0	10
0	1	1	1	11
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

0lp's

Y


0
0
0
0
0
0
0
0
0
0
0
0
1
1
1
1
1
1
1
1
1

1lp's sum &gt; 9, Y = 1

$s_3 s_2$	$s_3 s_0$	$b_1$	$b_0$	$c_0$
00	00	0	0	0
01	00	0	0	0
11	00	1	1	1
10	00	0	0	1


$$Y = AB + AC$$
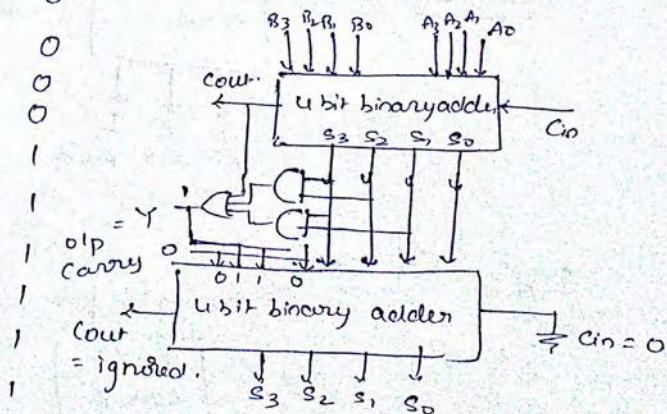
$$\text{i.e. } \Rightarrow s_3 s_2 + s_3 s_1$$



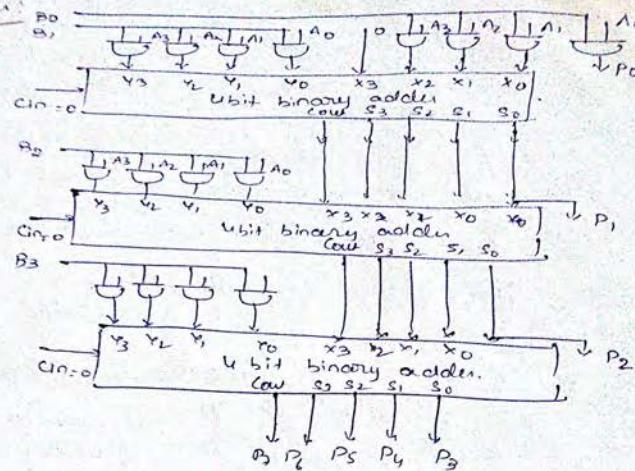
### Binary multiplier:

$A_3 A_2 A_1 A_0$   
 $B_3 B_2 B_1 B_0$   
 $A_3 B_0 A_2 B_0 A_1 B_0$   
 $= A_3 A_2 A_1 B_0 x$   
 $A_3 B_2 A_2 B_2 x$   
 $A_3 B_3 x$   
 $\dots P_2 P_1 P_0 A_0 B_0$   
 $P_0$




### Magnitude comparison:

Block dia:

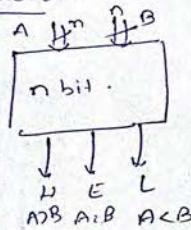

when  
 $H = 1 \Rightarrow A > B$   
 $E = 1 \Rightarrow A = B$   
 $L = 1 \Rightarrow A < B$

### Single bit comparison:

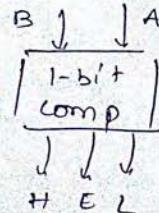

T-T


A	B	H	E	L
0	0	0	1	0
0	1	0	0	1
1	0	1	0	0
1	1	0	0	0

$$H = A\bar{B}$$



$$E = \bar{A}\bar{B} + A\bar{B} = \overline{A \oplus B}$$

$$L = \bar{A}B = \overline{AB} + A\bar{B}$$

Logic dia: A

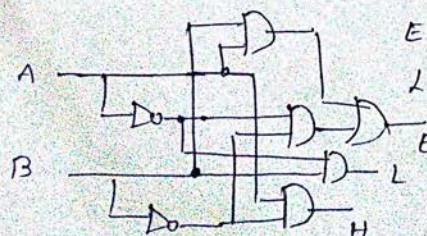

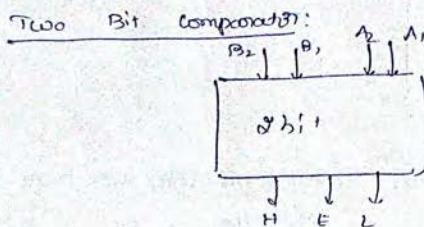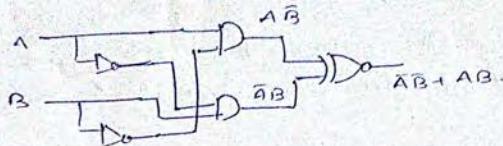19181 3, 5, 8, 15, 24, 37, 16  
39, 51, 57,  
64, 1.



K-map:

		B <sub>2</sub> B <sub>1</sub>	
		00	01
A <sub>2</sub> A <sub>1</sub>		00	00 01 11 10
00	00	00	00 01 11 10
01	01	01	01 10 00 01
10	10	10	10 11 00 00
11	11	11	11 01 01 00

$$H = A_2 \bar{B}_2 + A_2 \bar{A}_1 \bar{B}_2 + A_1 \bar{B}_2 \bar{B}_1$$

T.T	H E L
000	0 1 0 → 0
001	0 0 1 → 1
010	0 0 1 → 2
011	0 0 1 → 3
100	0 0 0 → 4
010	0 1 0 → 5
011	0 0 1 → 6
101	0 0 1 → 7
011	1 0 0 → 8
100	1 0 0 → 9
010	0 1 0 → 10
001	0 0 1 → 11
100	1 0 0 → 12
101	1 0 0 → 13
100	1 0 0 → 14
010	0 1 0 → 15

E	
1	0
0	1
0	0
0	0

$$E = \bar{A}_2 \bar{A}_1 \bar{B}_2 \bar{B}_1 + \bar{A}_2 A_1 \bar{B}_2 B_1 + A_1 A_2 B_1 B_2 + A_2 \bar{A}_1 + B_2 \bar{B}_1$$


Logic dia for H, E, L

0	1	1	1
0	0	1	1
0	0	0	0
0	0	1	0

$$L = \bar{A}_2 B_2 + \bar{A}_2 \bar{A}_1 B_1 + B_2 \bar{B}_1 \bar{A}_1$$
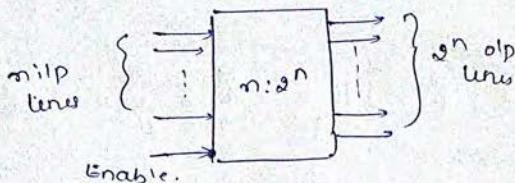
### Decoder:


converts an  $n$  bit binary ip lines into  $2^n$  o/p lines  
 i.e. only 1 o/p line is active for each one partihi-  
 lity.




represented by  $n \times m$  lines (i.e.  $n \times m$  lines)  
 $m = \text{ip's}$   
 $m = \text{o/p's}$

### 2 to 4 line decoder:

logic dia:

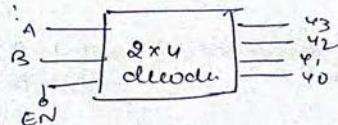

	ip's	o/p's	
EN	A B	$Y_0 \quad Y_1 \quad Y_2 \quad Y_3$	$Y_0 = \bar{A}\bar{B}$
0	0 X	0 0 0 0	$Y_1 = \bar{A}B$
1	0 0	1 0 0 0	$Y_2 = A\bar{B}$
1	0 1	0 1 0 0	$Y_3 = AB$
1	1 0	0 0 1 0	
1	1 1	0 0 0 1	

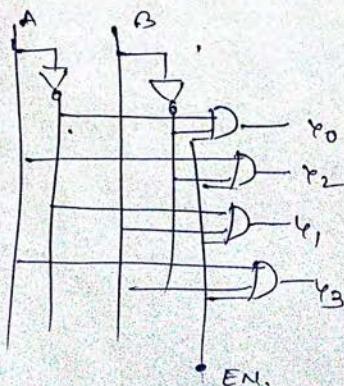


12.

### 3 to 8 line decoder:

3 ilp's

8 olp's

### 74x138 3 to 8 decoder:

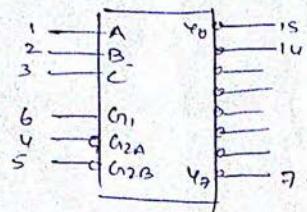


ilp's

	$G_{1B}$	$G_{2A}$	$G_1$	C	B	A
1	x	x	x	x	x	x
2	x	1	x	x	x	x
3	x	x	0	x	x	x
4	0	0	1	0	0	0
5	0	0	1	0	0	1

olp's


	$\bar{Y}_7$	$\bar{Y}_6$	$\bar{Y}_5$	$\bar{Y}_4$	$\bar{Y}_3$	$\bar{Y}_2$	$\bar{Y}_1$	$\bar{Y}_0$
1	1	1	1	1	1	1	1	1
2	1	1	1	1	1	1	1	1
3	1	1	1	1	1	1	1	1
4	1	1	1	1	1	1	1	1
5	1	1	1	1	1	1	1	0

### 74x139 Dual 2 to 4 decoder:

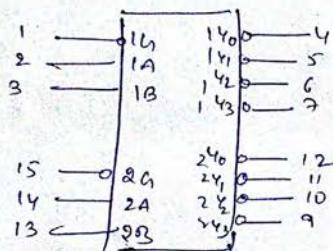


	$G_3$	$G_2$	$G_1$	$\bar{Y}_0$
1	x	x	x	1
2	0	0	0	1
3	0	0	1	1
4	0	1	0	0
5	0	1	1	0
6	1	1	0	0
7	0	1	1	1

### 4 to 16 using 2 to 4 decoders:

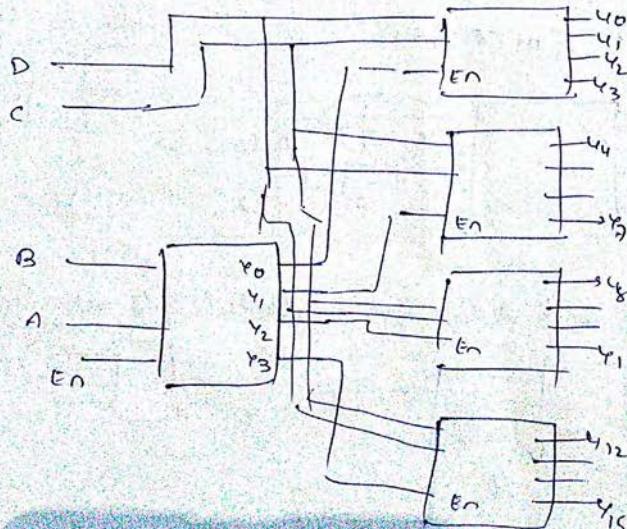

using 3708

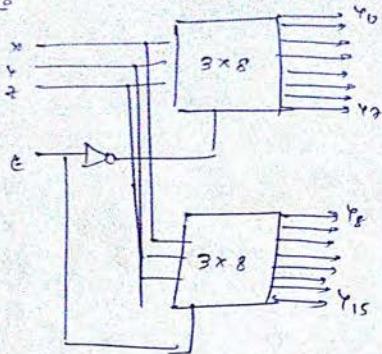


Realisation of multiple o/p funs using decoders:

→ To realise pos fun: Active high o/p.

$$\text{Ex: } F(A, B) = \overline{T}IM(0, 2, 3)$$

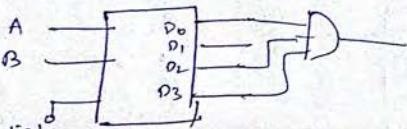using 2-to-4 decoder  
with active high o/p.



high o/p:

$\begin{matrix} 0 & 0 & 1 \\ 0 & 1 & 0 \\ 0 & 1 & 1 \end{matrix}$



$$F = (A + \bar{B} + C)(A + \bar{B} + \bar{C})(A + \bar{B} + \bar{C})$$

$$\text{Ex. } \therefore 1. \quad F_1(X, Y, Z) = \sum m(0, 1, 3, 7) \quad (\text{OR gate})$$



$$F_2(X, Y, Z) = \sum m(2, 3, 5)$$

$$\sum m(1, 2, 3)$$

for active low decod.

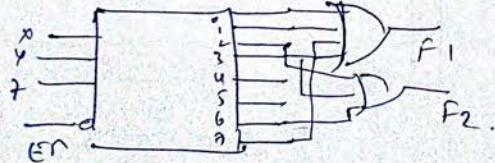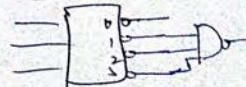

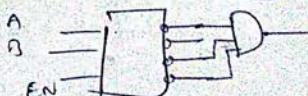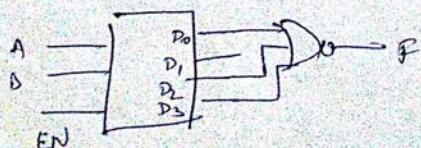Q.  $\overline{T}IM(0, 2, 3)$  using Active high decoder. for active low?




(12)

BCD to Decimal Decoder:

BCD code			Actual O/P.										$\bar{D}_{10} \text{ to } \bar{D}_{11} \text{ to } \bar{D}_{15}$	
$B_3$	$B_2$	$B_1$	$B_0$	$\bar{D}_0$	$\bar{D}_1$	$\bar{D}_2$	$\bar{D}_3$	$\bar{D}_4$	$\bar{D}_5$	$\bar{D}_6$	$\bar{D}_7$	$\bar{D}_8$	$\bar{D}_9$	None.
0	0	0	0	0	1	1	1	1	1	1	1	1	1	1
0	0	0	1	1	0	0	0	0	0	1	1	1	1	1
0	0	1	0	0	1	0	1	1	1	1	1	1	1	1
0	0	1	1	1	1	1	0	1	1	1	1	1	1	1
0	1	0	0	1	1	1	1	0	1	1	1	1	1	1
0	1	0	1	1	1	1	1	1	0	1	1	1	1	1
0	1	1	0	1	1	1	1	1	1	0	1	1	1	1
0	1	1	1	1	1	1	1	1	1	1	0	1	1	1
1	0	0	0	1	1	1	1	1	1	1	1	1	0	1
1	0	0	1	1	1	1	1	1	1	1	1	1	1	0
1	0	1	0	-	-	-	-	-	-	-	-	-	-	-
1	0	1	1	-	-	-	-	-	-	-	-	-	-	-
1	1	0	0	NONE										-
1	1	0	1	-	-	-	-	-	-	-	-	-	-	-
1	1	1	0	-	-	-	-	-	-	-	-	-	-	-
1	1	1	1	-	-	-	-	-	-	-	-	-	-	-


\* BCD to 7 Seg Decoder:

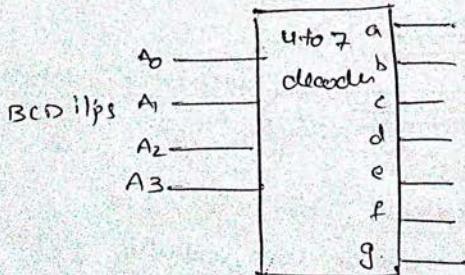


a  
f 1  
g 1  
e 1  
c  
d

decimal digit	B CD	seven seg. codes.
	A B C D A <sub>0</sub> A <sub>1</sub> A <sub>2</sub> A <sub>3</sub>	a b c d e f g
0	0 0 0 0	1 1 1 1 1 1 0
1	0 0 0 1	0 1 1 0 0 0 0
2	0 0 1 0	1 1 0 1 1 0 1
3	0 0 1 1	1 1 1 0 1 1 1
4	0 1 0 0	
5	1 0 0 1	
6	1 0 1 0	
7	1 0 1 1	
8	1 1 0 0	
9	1 1 0 1	

3) Common cathode type

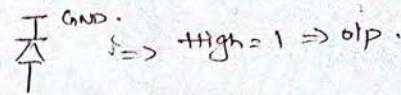

Common anode type

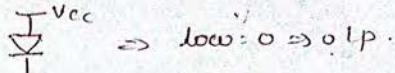

K-maps: cd  $\overline{cd}$  a

AB		cd		a	
		00	01	11	10
A <sub>0</sub> A <sub>1</sub>	00	1	0	1	1
	01	0	1	1	1
A <sub>0</sub> A <sub>1</sub>	11	X	X	X	X
	10	1	1	X	1

$$\begin{aligned} a &= A_0 + A_2 + A_1 A_3 + \bar{A}_1 \bar{A}_3 \\ &= A + C + B\bar{D} + \bar{B}\bar{D} \end{aligned}$$

$$-b : \bar{A}_1 + \bar{A}_2 \bar{A}_3 + A_2 A_3$$

$$= \bar{B} + \bar{C} \bar{D} + C D$$

$$c : B + \bar{C}$$


$$d : \bar{B}\bar{D} + C\bar{D} + B\bar{C}\bar{D} + \bar{B}C + A$$

$$e : \bar{B}\bar{D} + C\bar{D}$$

$$f : A + \bar{C}\bar{D} + B\bar{C} + B\bar{D}$$


$$g : A + B\bar{C} + \bar{B}C + C\bar{D}$$

Logic Dia!

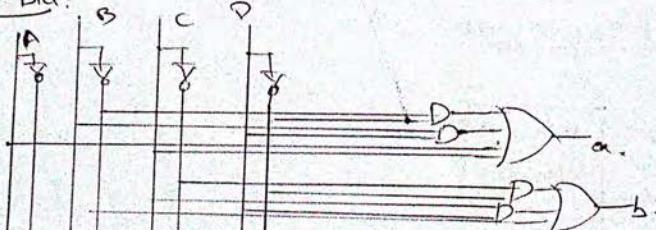


applications:

- used as code converters
- routing ip's to specified o/p's
- data distribution, (demux).
- switching fun.

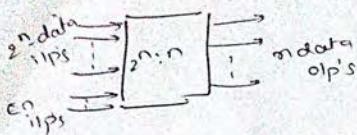Encoders:

Decimal to BCD Encoder ('It auxxlu?').

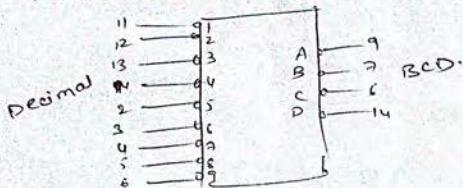

decimal	11ps	0	olp's
0	A B C D u s 5 6 7 8 9		B C B A.
0	1 1 1 1 1 1 1 1 1 1		1 1 1 1
1	0 1 1 1 1 1 1 1 1 1		1 1 1 0
2	x 0 1 1 1 1 1 1 1 1		
3	x x 0		

M to 2 Encoder:

A <sub>1</sub>	A <sub>2</sub>	A <sub>3</sub>	A <sub>4</sub>	Y <sub>0</sub>	Y <sub>1</sub>
0	0	0	1	1	1
A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>	Y <sub>1</sub>	Y <sub>0</sub>
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

$$Y_1 = \bar{A}_3 A_2 \bar{A}_1 A_0 + \\ A_3 \bar{A}_2 \bar{A}_1 \bar{A}_0$$

Priority encoders:

dis: If only 1 lfp is high  $\Rightarrow$  olp is correct in some case  
 & if more lfps might be high.

Ex: operating a key board, a person by releasing a key he may press the other so problem arises there.

Decimal to 8-bit priority encoder:

$D_0 D_1 D_2 D_3 D_4 D_5 D_6 D_7$	$A_3 A_2 A_1 A_0$
1 1 1 1 1 1 1 1	1 1 1 1
x x x x x x x 0	0 1 1 0
x x x x x x x 0 1	0 1 1 1
x x x x x x x 0 1 1	1 0 0 0

Octal to Binary priority encoder:

$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$	$A_3$	$A_2$	$C$
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0

Priority encoder:

Priority fun is included.

Ex: If 2(8) more lps = 1 at same time, l/p having highest priority will take precedence

4-bit priority encoder

l/p's				l/p's			V (Valid l/p indicator)
$D_0$	$D_1$	$D_2$	$D_3$	$Y_0$	$Y_1$	$Y_2$	
0	0	0	0	x	x	0	
1	0	0	0	0	0	1	
0	1	0	0	0	1	1	
0	0	1	0	1	0	1	
0	0	0	1	1	1	1	

$$Y_0 = D_3 + D_1 \bar{D}_2$$

$$Y_1 = D_2 + D_3$$

$$V = D_0 + D_1 + D_2 + D_3$$


(20)

MUX:



if p are 'n'

0/p = 1



Block dia:

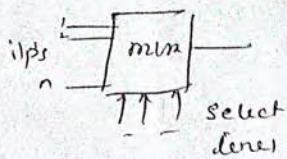

Functional dia:

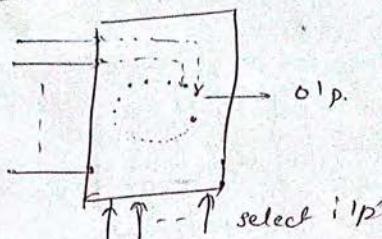
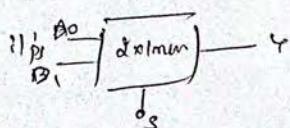
2x1 MUX:

S	A	B	Y
0	D0		D0
1		D1	D1

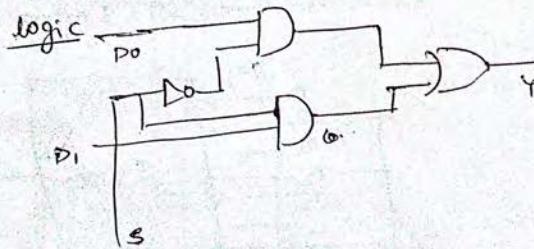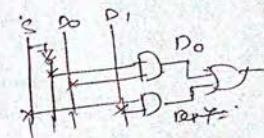

when  $S = 0$   
 $Y = D0$


when  $S = 1$   
 $Y = D1$

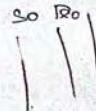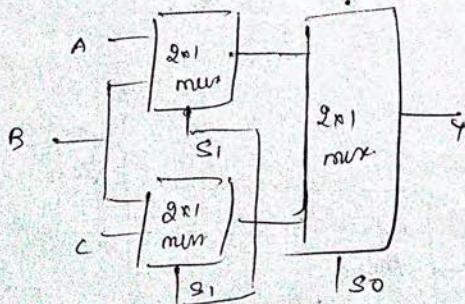3x1 MUX using 2x1 MUX


S0	S1	S	Y
0	0	0	D0
0	0	1	D1
0	1	0	D2
0	1	1	D3
1	0	0	D4
1	0	1	D5
1	1	0	D6
1	1	1	D7

S0	S1	S	A
0	0	0	D
0	0	1	B
1	0	0	C
1	1	1	D

UX1 min

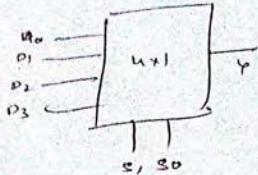

S0	S1	Y
0	0	D0
0	1	D1
1	0	D2
1	1	D3

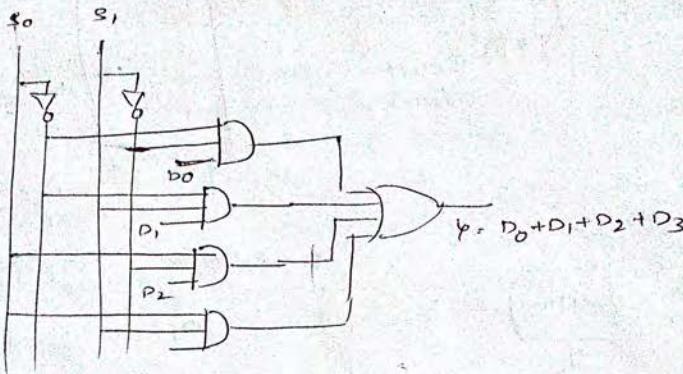


8x1 min

Ex: 1) Implement  $f = \sum m(1, 3, 5, 6)$  using 8x1 min.

7-7

EN	S	OP
E	S2 S1 S0	Y.
01	x x x	0
0	0 0 0	D0
0	0 0 1	D1
1		
1		
0	1 1 1	D3


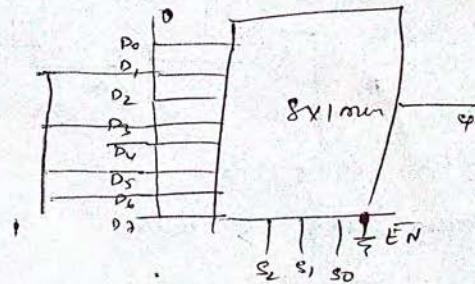


2)  $\sum m(1, 3, 5, 6)$

Implementation table:

A	D0	D1	D2	D3
A	0	1	2	3
A	1	1	1	1
A	1	0	1	0
A	0	0	0	1

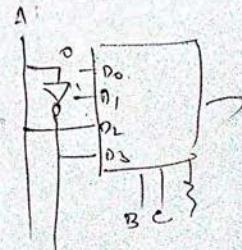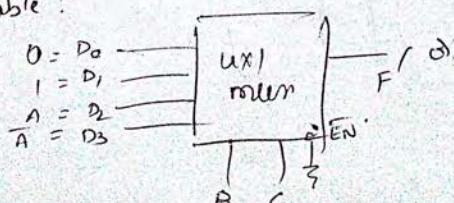
$$\begin{aligned} 0 &= D_0 \\ 1 &= D_1 \\ A &= D_2 \\ \bar{A} &= D_3 \end{aligned}$$




Ex1 mux  $\Sigma m(0,1,3,4,8,9,15)$

	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	D <sub>4</sub>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>
A	0	1	2	3	4	5	6	7
B	8	9	10	11	12	13	14	15
	1	1	A	A	A	A	A	

Ex2 Tim(2,5,6,7,10,11,12,13,14)

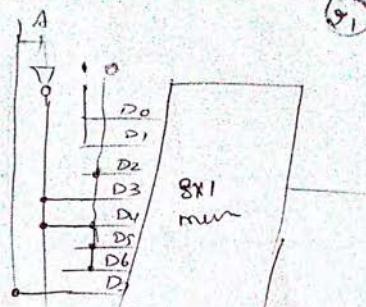

- app:
- 1. 7 seg display
  - 2. logic fun gen
  - 3. Digital counter
  - 4. operating sequencing
  - 5. Data selection, switching
  - 6. parallel & serial conversion
  - 7. code generation.
- De morgan's: logic dia:

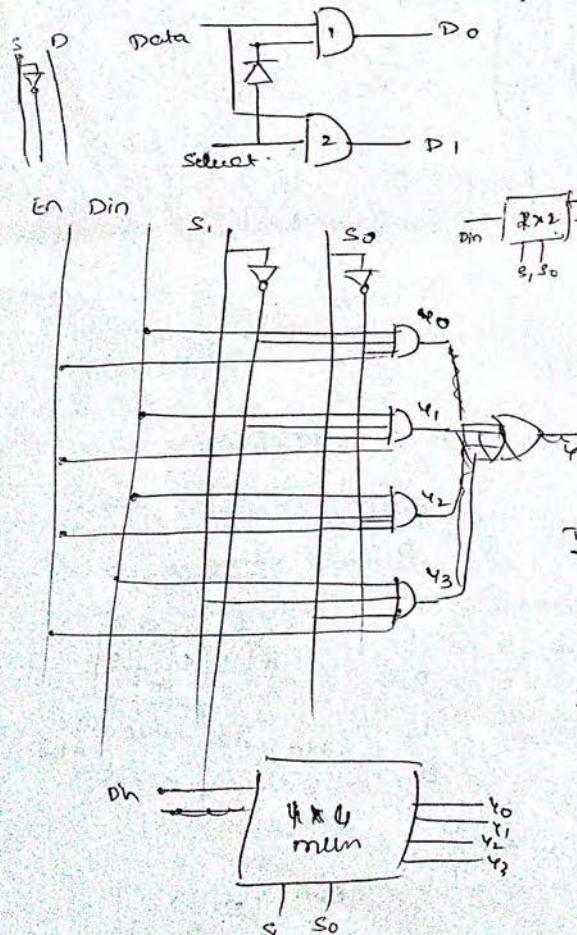



Ex3: Implement F-S using elemen

T-T F-P

	A	B	C	D	B <sub>0</sub>
0	0	0	0	0	0
1	0	0	1	1	1
2	0	1	0	1	1
3	0	1	1	0	1
4	1	0	0	1	0
5	1	0	1	0	1
6	1	1	0	0	0
7	1	1	1	1	1

$$B = \Sigma m(1, 2, 4, 7)$$

$$B_0 = \Sigma m(1, 2, 3, 5, 7)$$

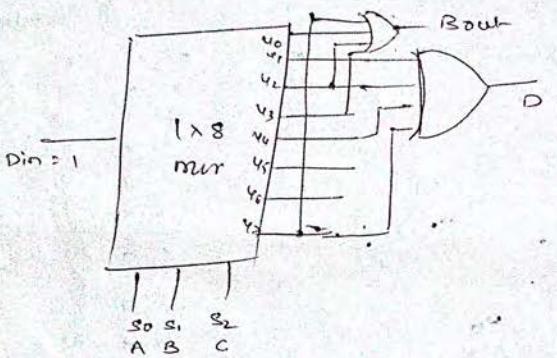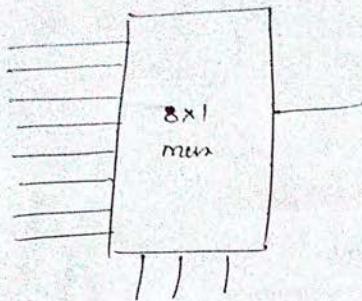

### Parity checker/generator:

TI of parity generator for even & odd parity

A	B	C	Odd	Even
0	0	0	1	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	0	1

K-map:

	B̄C	BC	BC̄	BC̄
Ā	1	0	1	0
A	0	1	0	1

$$\text{P}_{\text{odd}}: \bar{A}\bar{B}\bar{C} + A\bar{B}C + \bar{A}B\bar{C} + AB\bar{C}$$

$$\Rightarrow \bar{C}(A \oplus B) + C(CA \oplus B)$$


$$\Rightarrow (A \oplus B) \oplus C$$

	0	1	0	1
1	0	1	0	1

$$\text{P}_{\text{even}}: A\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}C + A\bar{B}C$$

$$\Rightarrow (A \oplus B) \oplus C.$$

logic dia:

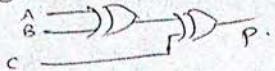

7.7 Q3 Even parity checker:

ubits received

A B C D

0 0 0 0

0 0 0 1

0 0 1 0

0 0 1 1

0 1 0 0

0 1 0 1

0 1 1 0

0 1 1 1

1 0 0 0

1 0 0 1

1 0 1 0

1 0 1 1

1 1 0 0

1 1 0 1

1 1 1 0


1 1 1 1

parity error check.

PEC.

0	1	0	1
1	0	1	0
0	1	0	1
1	0	1	1
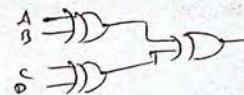
$$\text{PEC} = (A \oplus B) \oplus (C \oplus D)$$



code converter:

Binary to BCD converter:

Binary  
D C B A

0 0 0 0

0 0 0 1

0 0 1 0

⋮

1 0 0 1

1 0 1 0

1 0 1 1

BCD code.  
B<sub>4</sub> B<sub>3</sub> B<sub>2</sub> B<sub>1</sub> B<sub>0</sub>

0 0 0 0 0

0 0 0 0 1

0 0 0 1 0

⋮

0 1 0 0 1

1 0 0 0 0

1 0 0 0 1

K-map.

$$B_4 = DC + DB$$

$$B_3 = D\bar{C}$$

$$B_2 = \bar{D}C + CB$$

$$B_1 = DC\bar{B} + \bar{D}B$$

$$B_0 = A$$

Logic dia:

BCD to Binary:

BCD				Binary			
B <sub>4</sub>	B <sub>3</sub>	B <sub>2</sub>	B <sub>1</sub>	E	D	C	A
0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
1	0	0	0	0	1	0	1
1	0	0	1	0	1	0	1
1	0	1	0	1	1	1	1
1	0	1	1	1	0	0	0
1	0	1	0	1	0	0	1

Variable K-map:

$$+3(A \cdot 2B_0)$$

$$B_4 = 1$$

$$B_4 = 0$$

$$\begin{array}{c} B_3 \\ \diagup \\ B_3 B_2 \\ \diagdown \\ B_2 B_0 \end{array}$$

$$B = B_3 \oplus B_4$$

$$C = \overline{B_4} B_2 + B_2 \overline{B}_1 + B_4 \overline{B}_2 B_1$$

$$D = \overline{B_4} B_3 + B_4 \overline{B}_3 \overline{B}_2 + B_4 \overline{B}_3 B_2$$

$$E = B_4 B_3 + B_4 B_2 B_1$$

Logic dia:

BCD to Excess-3:

Decimal	BCD	Excess-3
	B <sub>3</sub> B <sub>2</sub> B <sub>1</sub> B <sub>0</sub>	E <sub>3</sub> E <sub>2</sub> E <sub>1</sub> E <sub>0</sub>
0	0 0 0 0	0 0 1 1
0	0 0 0 0	0 0 0 0
1	0 0 0 1	1 1 0 0
1	1 0 0 1	1 1 0 0
9	1 0 0 1	1 1 0 0

K-map:

$$E_3 = B_3 \oplus B_2 (B_0 + B_1)$$

$$E_2 = B_2 \bar{B}_1 \bar{B}_0 + \bar{B}_2 (B_0 + B_1)$$

$$E_1 = B_1 \oplus B_0$$

$$E_0 = \bar{B}_0$$

Logic dia:

Excess-3 to BCD code converter

		B <sub>3</sub>	B <sub>2</sub>	B <sub>1</sub>	B <sub>0</sub>		
E <sub>3</sub>	E <sub>2</sub>	E <sub>1</sub>	E <sub>0</sub>	0	0	0	0
0	0	1	1	0	0	0	1
0	1	0	0	0	0	1	0
⋮	⋮	⋮	⋮	⋮	⋮	⋮	⋮

K-map:

$$B_0 = \bar{E}_0$$

$$B_1 = E_1 \oplus E_0$$

$$B_2 = \bar{E}_2 \bar{E}_1 + E_2 E_1 E_0 + E_3 E_1 \bar{E}_0$$

$$B_3 = E_3 E_2 + E_3 E_1 E_0$$

Logic dia:

Binary to Gray code:

Binary				Gray			
B <sub>3</sub>	B <sub>2</sub>	B <sub>1</sub>	B <sub>0</sub>	G <sub>3</sub>	G <sub>2</sub>	G <sub>1</sub>	G <sub>0</sub>
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
⋮	⋮	⋮	⋮	⋮	⋮	⋮	⋮

K-map:

$$\begin{aligned}G_0 &= B_0 \oplus A \\ G_1 &= C \oplus B \\ G_2 &= D \oplus C \\ G_3 &= D\end{aligned}$$

Logic dia:

Binary code to Gray code:

Gray code	Binary
$G_3 G_2 G_1 G_0$	$B_3 B_2 B_1 B_0$

$$A = (G_3 \oplus G_2) \oplus (G_1 \oplus G_0)$$

$$B = G_3 \oplus G_2 \oplus G_1.$$

$$C = G_3 \oplus G_2$$

$$D = G_3.$$

Logic dia:

BCD to Gray code

$$B_3 B_2 B_1 B_0 \quad G_3 G_2 G_1 G_0.$$

$$G_0 = B_1 \oplus B_0$$

$$G_1 = B_2 \oplus B_1$$

$$G_2 = B_2 + B_3$$

$$G_3 = B_3.$$

Logic dia:



Hazards:

The uncontrolled switching transients that may appear at the o/p of a celts are Hazards.

These occur bcz of prop delays., they occur in combinational celts.

Hazards in combinational celts:

Ex:

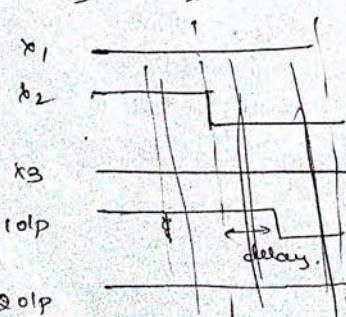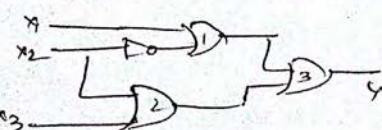

static-1 hazard.


$\Rightarrow$  o/p is 0, but should be 1.

static-0:

o/p is 1, but should be 0

Dynamic:

changes continuously.

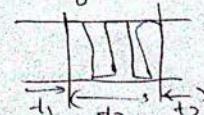

(Q5)

Hazard free realization: too far from static.

- Hazards can be eliminated by enclosing two minterms /

two max terms in gues.

Ex:  $f_2 = x_1x_2 + \bar{x}_2x_3$ . add one more minterm  $x_1x_3$ .

eliminating hazard:

$x_1$	$x_2$	$x_3$	$\bar{x}_1$	$\bar{x}_2$	$\bar{x}_3$
0	0	0	1	1	1
0	0	1	1	0	0
0	1	0	1	0	1

$$f_2 = x_1x_2 + \bar{x}_2x_3$$

0	0
1	1

$$y_2 = x_1x_2 + \bar{x}_2x_3 + x_1x_3$$

Ex:  $f_2 = \Sigma m(1, 3, 6, 7, 13, 15)$

obtain hazard free clt:

	$\bar{C}D$	$\bar{C}D$	$CD$	$CD$
$\bar{A}\bar{B}$	0	1	1	0
$\bar{A}B$	0	0	1	1
$A\bar{B}$	0	1	1	0
$AB$	0	0	0	0

$$f_2 = \bar{A}\bar{B}D + CD\bar{A} + \bar{A}BC + BCD + ABD.$$

Essential hazards:

In Asynchronous seq clt., the hazard caused by unequal delays along two (or) more paths that come from same ilp.

Ex:  $\Sigma m(0, 2, 6, 7, 8, 10, 12)$ , find Hazard free realization.

	$\bar{C}D$	$\bar{C}D$	$CD$	$CD$
$\bar{A}\bar{B}$	1	1	1	1
$\bar{A}B$	1	1	1	1
$A\bar{B}$	1	1	1	1
$AB$	1	1	1	1

$$f_2 = \bar{B}D + \bar{A}BC + A\bar{C}D + \bar{A}CD$$

Hazard free fun:

$$f_2 = \bar{B}D + \bar{A}BC + A\bar{C}D + \bar{A}CD$$

Note: static & dynamic hazards occur both in combinational sequential cells

Essential  $\rightarrow$  yard occur in only sequential cat

Functional hazard: 

## \* code converters:

